

To check if any circuit decomposition is correct you can use 2 methods:

Suppose we are trying to implement an n (say, $n=1$ here) qubit gate C using its decomposition, i.e.



To check if its correct you can:

(Easier method & faster in some cases but not the best for beginners as using analytical method will help you learn more about gate algebra)

(i) See the output for all the 2^n basis vectors, if each gives the expected output then the circuit is correct as any state is a linear combination of these basis vectors & any gate is a linear operator.

(Analytical method, faster in some cases)

(ii) Calculate if $BA = C$ analytically.

For your question, the decomposition contains CNOT, H, T & S gate

Now, for 3 qubit circuit

$$CNOT_{1 \rightarrow 1} \equiv |0X0\rangle \otimes I \otimes I + |1X1\rangle \otimes X \otimes I$$

$$\equiv |0X0\rangle \otimes (|0X0\rangle + |1X1\rangle) \otimes (|0X0\rangle + |1X1\rangle) \\ + |1X1\rangle \otimes (|0X1\rangle + |1X0\rangle) \otimes (|0X0\rangle + |1X1\rangle)$$

(Try to reason why this is correct)

$$H_3 = I \otimes I \otimes (|1+X0\rangle + |1-X1\rangle)$$

$$T_1 = \begin{bmatrix} 1 & 0 \\ 0 & e^{i\frac{\pi}{4}} \end{bmatrix} \equiv |0X0\rangle \otimes I \otimes I + e^{i\frac{\pi}{4}} |1X1\rangle \otimes I \otimes I$$

$$S_2 = \begin{bmatrix} 1 & 0 \\ 0 & i \end{bmatrix} \equiv I \otimes (|0X0\rangle + i|1X1\rangle) \otimes I$$

The subscript A_n denotes A is acting only on n^{th} qubit. I have given representation for specific n 's, adjust the repre -- as n changes yourself

Now that you know outer product representation of the required gates,

do the $BA = C$ method & see if the the decomposition is correct.